

```

1  /*
2   Caitlin DeShazo-Couchot and Ashley Guillard
3   EE 271 Au23: Professor Hussein
4   November 9, 2023
5   Lab 4: LED2, LED3, LED4, LED6, LED7, LED8
6  */
7
8  // Handles the normal LEDs during the game of Tug-of-War.
9  // Inputs: CLOCK, Reset, Left Button, Right Button, Left Light, and Right Light.
10 // Outputs: The state of the LED this is referring to, either On or Off.
11 module normalLight (CLOCK, Reset, L, R, NL, NR, lightOn);
12
13     // INPUT LOGIC
14     input logic CLOCK, Reset;
15
16     // GAME LOGIC
17     // L is true when left key is pressed, R is true when the right key is pressed.
18     // NL is true when the light on the left is on, and NR is true when the light on the
right is on.
19     input logic L, R, NL, NR;
20
21     // OUTPUT LOGIC: When lightOn is true, the normal light should be on.
22     output logic lightOn;
23
24
25     // State Variables
26     enum logic [1:0] { OFF, ON } ps, ns;
27
28     // Next State Logic
29     always_comb begin
30         case (ps)
31             OFF:
32                 if ((NL & R & ~L) | (NR & L & ~R))
33                     ns = ON;
34                 else
35                     ns = OFF;
36             ON:
37                 if ((R & ~L) | (L & ~R))
38                     ns = OFF;
39                 else
40                     ns = ON;
41         endcase
42     end
43
44     // Output Logic
45     always_comb begin
46         case (ps)
47             OFF:
48                 lightOn = 1'b0;
49             ON:
50                 lightOn = 1'b1;
51         endcase
52     end
53
54     // DFFs
55     always_ff @(posedge CLOCK) begin
56         if (Reset)
57             ps <= OFF;
58         else
59             ps <= ns;
60     end
61 endmodule
62
63 //Tests all possible combinations for the normalLight
64 module normalLight_testbench();
65
66     // Test inputs and outputs
67     logic CLOCK, Reset, L, R, NL, NR;
68     logic lightOn;
69
70     // Instantiate the hazard_lights module
71     normalLight dut (.CLOCK, .Reset, .L, .R, .NL, .NR, .lightOn);
72
73     //CLOCK setup
74     parameter CLOCK_period = 10;
75

```

```
76     initial begin
77         CLOCK <= 0;
78         forever #(CLOCK_period) CLOCK <= ~CLOCK;
79     end //initial
80
81     // Test cases for Tug of War game
82     initial begin
83         Reset <= 1;
84         Reset <= 0;      L = 0; R = 0; NL = 0; NR = 0; @(posedge CLOCK); //Reset
85                             NR = 1; @(posedge CLOCK);
86                             NL = 1; NR = 0; @(posedge CLOCK);
87                             NR = 1; @(posedge CLOCK);
88                             R = 1; NL = 0; NR = 0; @(posedge CLOCK);
89                             NR = 1; @(posedge CLOCK);
90                             NL = 1; NR = 0; @(posedge CLOCK);
91                             NR = 1; @(posedge CLOCK);
92                             L = 1; R = 0; NL = 0; NR = 0; @(posedge CLOCK);
93                             NR = 1; @(posedge CLOCK);
94                             NL = 1; NR = 0; @(posedge CLOCK);
95                             NR = 1; @(posedge CLOCK);
96                             R = 1; NL = 0; NR = 0; @(posedge CLOCK);
97                             NR = 1; @(posedge CLOCK);
98                             NL = 1; NR = 0; @(posedge CLOCK);
99                             NR = 1; @(posedge CLOCK);
100
101         $stop;
102     end //initial
103 endmodule
```