```
2
3
         Caitlin DeShazo-Couchot and Ashley Guillard
         EE 271 Au23: Professor Hussein
November 9, 2023
 4
 5
6
7
         Lab 4: Victory Logic
      // Handles the Victory Case for HEXO where 1 is displayed for Player 1 and 2 for Player 2.
      // Inputs: CLOCK, Reset, Left Button, Right Button, Left Light, and Right Light. // Outputs: The state of the LED this is referring to, either On or Off.
 8
 9
10
     module victory (CLOCK, Reset, L, R, LEDR9, LEDR1, HEX0);
11
12
           // INPUT LOGIC
13
           input logic CLOCK, Reset, L, R, LEDR9, LEDR1;
14
15
           // OUTPUT LOGIC
16
17
           output logic [6:0] HEXO;
18
           enum { P1, P2, NONE } ps, ns;
19
20
21
22
23
24
25
26
27
28
29
30
31
32
33
           // Combinational Logic
           always_comb begin
                case (ps)
                    P1: ns = P1;
P2: ns = P2;
                    NONE:
                        if (L == 1 \&\& R == 0 \&\& LEDR1 == 1)
                            ns = P1;
                        else if (L == 0 \&\& R == 1 \&\& LEDR9 == 1)
                            ns = P2;
                            ns = NONE;
                 endcase
           end
34
35
           // Output Logic
           always_comb begin
36
             Case (ps)
P1: HEX0 = 7'b0100100;
37
38
                 P2: HEXO = 7'b1111001;
39
40
                 41
             endcase
42
         end
43
44
          // Sequential Logic
         always_ff @(posedge CLOCK) begin
45
             if (Reset)
46
47
                 ps <= NONE;
48
             else
49
                 ps \ll ns;
50
         end
51
52
      endmodule
53
```